


Code No: 123BR

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year I Semester Examinations, September - 2021****BASIC ELECTRICAL ENGINEERING****(Common to CSE, IT)****Time: 3 hours****Max. Marks: 75**

Answer any five questions
All questions carry equal marks

- - -

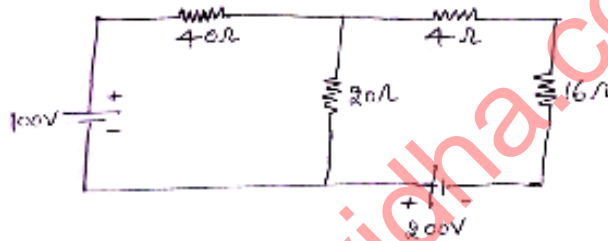- 1.a) State and explain Maximum Power transfer theorem.
 b) Find the current in the resistors $R_1 = 10\Omega$ and $R_2 = 20\Omega$ connected in parallel across a voltage source. The supply current is 50 A. Also, find power across each resistance. [8+7]
2. Using Super position theorem, find the current through the 20Ω resistor for the network shown below: [15]



- 3.a) Explain the terms with respect to Alternating Quantity:
 i) Instantaneous value and ii) Time period.
 b) If the form factor of a current waveform is 2 and the amplitude factor is 2.5, find the average value of the current if the maximum value of the current is 500 A. [8+7]
- 4.a) Explain the terms with respect to Alternating Quantity:
 i) average value ii) Root mean square value iii) Maximum value.
 b) A 230 V, 50 Hz voltage is applied to a coil $L = 5$ H and $R = 2\Omega$ is in series with a capacitance C. What value must C have in order that the voltage across the coil is 400 V? [8+7]
- 5.a) Derive the expression of emf induced in a transformer.
 b) Explain the working of transformer on lagging power factor load with a neat phasor diagram. [8+7]
- 6.a) Explain the various constructional features to be considered for a single phase transformer.
 b) In a 25 KVA, 2000/200 V transformer the iron and full load copper losses are 350 W and 400 W respectively. Find the efficiency at 0.8 power factor lagging at i) Full load and ii) Half load. [7+8]
- 7.a) Derive the emf equation of a dc generator.
 b) Explain the working of a 3-phase Induction Motor. [7+8]
8. Explain the working of Attraction type moving iron instrument with a neat sketch. [15]

---ooOoo---