

Code No: 123BR

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, April/May - 2023

BASIC ELECTRICAL ENGINEERING

(Common to CSE, IT)

Time: 3 Hours

Max. Marks: 75

Note: i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, Answer all questions.


iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART- A**(25 Marks)**

- 1.a) Define Kirchoff's current law. [2]
- b) What are the types of sources? Give examples. [3]
- c) Define form factor of a sinusoidal waveform. [2]
- d) What is J operator? Explain its significance. [3]
- e) Define leakage flux. [2]
- f) Define eddy current loss. How to reduce this in a single phase transformer? [3]
- g) What is slip of 3-phase induction motor? [2]
- h) What is a DC series motor? Draw the circuit diagram of dc series motor. [3]
- i) What is the need for damping torque in measuring instrument? [2]
- j) List out various instruments used to measure voltage, current and power. [3]


PART-B**(50 Marks)**

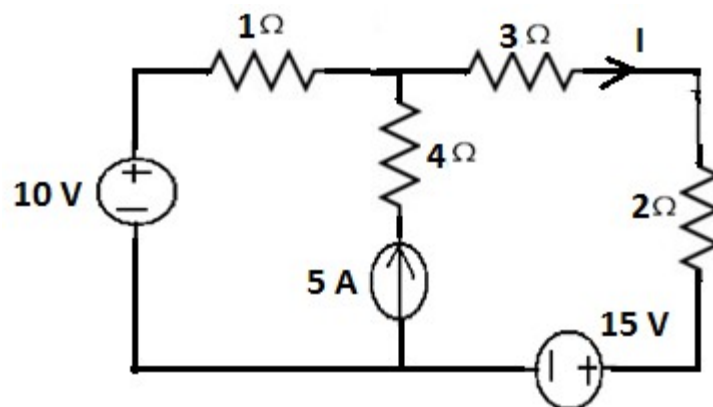- 2.a) Discuss in detail about the star to delta conversion of resistive circuits in the suitable example.
- b) Using thevenin's theorem, find the current 'I' in the circuit below. [5+5]



OR

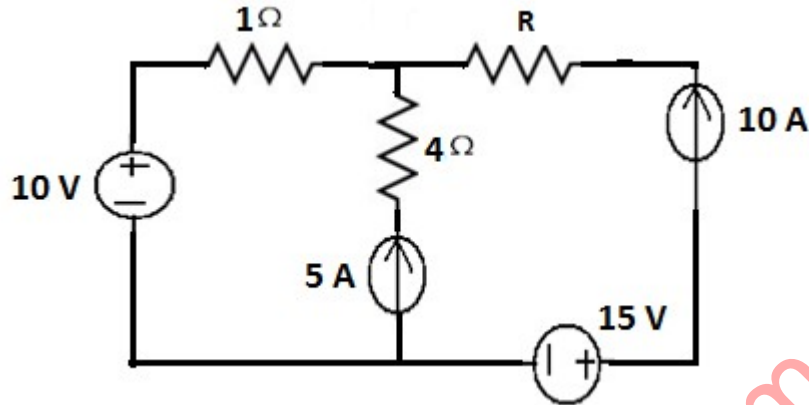- 3.a) State and explain superposition theorem.
 b) Find the maximum power delivered to the load resistor 'R' using maximum power transfer theorem. [5+5]




- 4.a) Derive the expression for average value and form factor of a sinusoidal waveform whose amplitude is A and whose time period is T.
 b) Simplify the following expression [5+5]
 $1\angle 0^\circ + 2\angle 90^\circ + 3\angle -90^\circ$

OR

- 5.a) Derive an expression for current flowing through a capacitor when it is subjected by A.C source of $v = V_m \sin \omega t$.
 b) Find the impedance and current of R-L series circuit having $R=10\ \Omega$; $L=50\ \text{mH}$ connected across 230V, 50Hz supply. [5+5]
- 6.a) Explain the constructional details of single phase transformer
 b) A 10 KVA single phase transformer has an efficiency of 98% at Full Load and also at Half Load. The power factor is unity in both cases. Find the efficiency of the transformer at 70% Load. [5+5]

OR

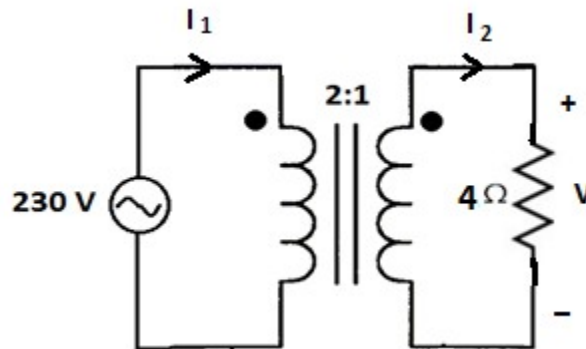- 7.a) Derive the expression for the voltage regulation of single phase transformer for lagging load
 b) For the ideal transformer shown below, find the currents I_1 , I_2 and V. [5+5]



- 8.a) Explain the principle of operation of DC generator.
 b) Discuss in detail about different losses in DC motors. [5+5]

OR

- 9.a) Discuss in detail about the working of three phase induction motor.
 b) Obtain the torque equation of d.c motors. [5+5]

- 10.a) Give the detailed classification of instruments.
b) Explain the working of moving iron voltmeter. [5+5]

OR

- 11.a) Explain the basic working principle of Permanent Magnet Moving Coil (PMMC) instruments.
b) What are the advantages and limitations of Permanent Magnet Moving Coil (PMMC) instruments? [5+5]

--ooOoo--

downloaded from
StudentSuvidha.com