

Code No: 154AE

**R18**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B. Tech II Year II Semester Examinations, April/May - 2023**

**BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**

**(Common to CE, ME, MMT, MIE)**

**Time: 3 Hours**

**Max. Marks: 75**

**Note:** i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, Answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**PART – A**


**(25 Marks)**

- 1.a) Define active and passive elements. [2]
- b) What is node in an electrical circuit? Draw example circuit and indicate nodes. [3]
- c) What are the different types of wires? [2]
- d) What is the function of fuse? [3]
- e) What is the principle of DC generator? [2]
- f) What are the losses in transformer and how to minimize? [3]
- g) Define Ripple Factor. [2]
- h) What is the need for rectifier? [3]
- i) What do you mean by biasing FET? [2]
- j) What are the types of BJT? Draw the symbols of each one. [3]

**PART – B**

**(50 Marks)**

- 2.a) Determine the unknown voltage.

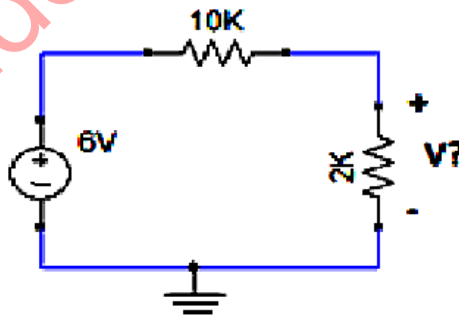

- b) Derive Average and RMS values of AC voltage. [4+6]

**OR**

- 3.a) Determine the unknown current  $I$  through the node, which is connected with 3 more branches in which two branch currents are 4A and 6A flowing towards the junction and third branch current 2A is flowing away from node.
- b) Analyze RL Series circuit excited by A.C. source with necessary diagrams and equations. [4+6]

4. Explain about various types of batteries and write important characteristics for batteries. [10]

**OR**

5. With necessary diagrams, explain various components of L.T. switch gear. [10]

6. Explain the construction details and working of single-phase transformer and list the applications of transformer. [10]

**OR**

7. Derive the EMF equation of DC generator. [10]

8. Explain the V-I Characteristics of p-n junction diode. [10]

**OR**

9. Explain the operation of full wave bridge rectifier with relevant circuit and Waveform. [10]

10. With neat diagrams, contrast CE, CB, and CC configurations of a BJT. [10]

**OR**

11. Explain the construction details, principle and working of FET. [10]

---ooOoo---

downloaded from  
StudentSuvidha.com