

Roll No.

Total Pages : 03

BCA/M-19

19004

LOGICAL ORGANIZATION OF
COMPUTERS
BCA-104

Time : Three Hours]

[Maximum Marks : 80

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. Q. No. 1 is compulsory.

Compulsory Question

1. (a) Define Unicode.
- (b) Draw Venn Diagram for A or \bar{B} .
- (c) What do you mean by Basic Gates ?
- (d) Define a decoder.
- (e) What do you mean by a Sequential Circuit ?
- (f) What is a Shift Register ?
- (g) Define Cache Memory.
- (h) Fill in the blanks :

1 TB =KB.

2×8

Unit I

2. Evaluate the following :
- (a) $(53.25)_{10} = (?)_2$
 - (b) $(11011.01)_2 = (?)_{10}$
 - (c) $(63.27)_8 = (?)_{10}$
 - (d) $(195.75)_{10} = (?)_{16}$
3. (a) What do you mean by Boolean Algebra ? 4
- (b) Write down the postulates of Boolean Algebra. 12

Unit II

4. (a) Introduce XOR and XNOR gates. 3×2
- (b) Perform NAND Gate implementation for :
- (i) $A.\bar{B} + A.B.C + \bar{A}.B.\bar{C}$
 - (ii) $(\bar{A} + B).(A + B + \bar{C}).(\bar{A} + \bar{B} + C)$
5. (a) Define Half Adder and Full Adder. 3×2
- (b) Design a Combinational Circuit for a full subtractor. 10

Unit III

6. Explain the working of SR Flip-Flop in detail. 16
7. Design a Mod-9 Counter. 16

L-19004

2

Unit IV

8. (a) What do you mean by the term Memory ? 4
- (b) Describe the different memory parameters. 12
9. (a) What is an Instruction format ? 6
- (b) Explain DMA transfer in detail. 10

(2-17/11)L-19004

3

150