

BT-4 / M-19
ANALOG ELECTRONICS
Paper-ECE-208 N

Time allowed : 3 hours]

[Maximum marks : 75

Note : Attempt any five questions selecting at least one from each unit.

Unit-I

1. (a) Why does gain of an amplifier falls off at low and high frequencies? 7
- (b) Explain voltage divider biasing for BJT. 8
2. (a) What is operating point of an amplifier? What factors are to be considered for selecting the Q point for an amplifier? 10
- (b) Compare JFET and MOSFET. 5

Unit-II

3. (a) Compare class A power amplifier with class B and class C power amplifiers. 7
- (b) Explain the working of two stage RC-coupled amplifier. 8
4. What is feedback? Explain the two types of feedback. An amplifier with negative feedback has a voltage gain of 100. It is found that without feedback an input signal of 50mV is required to produce a given output, whereas with feedback, the input signal must be 0.6V for same output. Calculate the value of A and β . 15

Unit-IV

7. Discuss dual input and balanced output differential amplifier configuration of Op-Amp. Calculate its input resistance, output resistance and CMRR. 15
8. (a) Explain the working of Schmitt trigger. 7
- (b) Define CMRR, slew rate, common mode gain, differential mode gain. 8