

Roll No.

Total Pages : 03

BT-4/M-20

34009

DIGITAL ELECTRONICS

EE-204-E


Time : Three Hours]

[Maximum Marks : 100

Note Attempt Five questions in all, selecting at least one question from each Unit.

Unit I

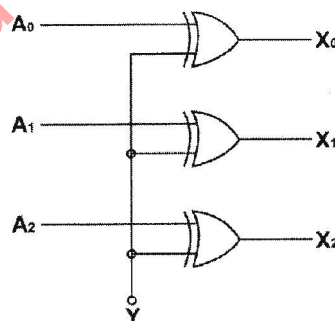1. (a) If $(211)_x = (152)_8$ find the value of x .
(b) Subtract 79.625 from 27.125 using 12 bit 2's complement method.
(c) Convert $(4057)_{16}$ Hexadecimal.
(d) Add $1010.11 + 1101.10 + 1001.11 + 1111.11$.
(e) What should be the value of Y so that X is complement of A_0 . Explain the reason for your answer. **5×2=10**




(2)L-34009

1

2. (a) Show that : 5

$$\bar{A}\bar{B}C + B + \bar{B}D + \bar{A}B\bar{D} + AC = B + C$$

(b) Draw the simplest possible logic diagram that implements the output of the logic diagram shown below : 5

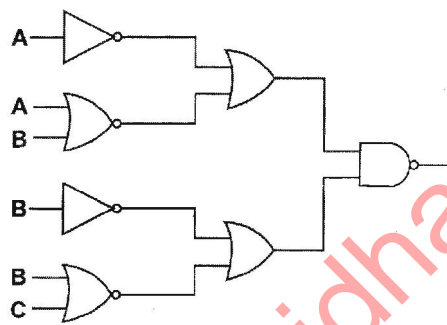

Unit II

3. (a) Reduce the function using Q-M method : 6

$$S(A, B, C, D) \sum (0, 1, 2, 3, 5, 6, 8, 9, 10, 11, 13, 14)$$

(b) Explain parity generator. 4

4. (a) Prepare a K-map and write the expression in SOP form from the K-map for the following expression : 5

$$(A + B + \bar{C} + \bar{D})(\bar{A} + C + \bar{D})(\bar{D} + A + B + \bar{C}) + D$$

$$(\bar{B} + \bar{C})(\bar{B} + \bar{C})(A + \bar{B})(\bar{B} + \bar{D})$$

(2)L-34009

2

- (b) Implement the following function using 8 : 1 MUX :
 $F = \sum(0, 1, 3, 6, 8, 9, 10, 12, 13, 14)$

Unit III

5. (a) Convert a S-R flip-flop to J-K flip-flop. **5**
 (b) Draw the logic and timing diagrams for SISO, shift right register for data input 1010. **5**
6. (a) Design a 4-bit weighted resistor DAC whose full scale output voltage is (+5 V). The logic levels are I = +5 V and O = 0 V. Find the output voltage for input 1101. **5**
 (b) What is the difference between up and down counter? Design a MOD 13 counter and draw its neat diagram. **5**

Unit IV

7. (a) What is interfacing of two logic families? Explain it with the help of CMOS driving TTL logic family. **5**
 (b) What is a logic family? Classify the important ones. **5**
8. (a) State the difference between ROM, PROM, EPROM and EEPROM. **5**
 (b) What is PLA? Describe its uses. **5**

(2)L-34009

3

—