

Roll No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 18

**B.Tech.(EE) PT (Sem.-3)**  
**DIGITAL ELECTRONICS**  
Subject Code : BTEE-404  
M.Code : 72164

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTION TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

**SECTION-A**

Answer briefly :

- 1) Convert Decimal Number 4587 into Octal and Hexadecimal Number systems.
- 2) Subtract 21 from 36 using 2's complement method.
- 3) State and prove Demorgan's Theorem.
- 4) Convert  $AB + A\bar{B}$  into POS form.
- 5) Define MOD counters.
- 6) Draw a VHDL view of a Digital model.
- 7) What do you mean by Figure of merit in Logic family?
- 8) Define accuracy of D/A converters.
- 9) Differentiate between RAM and ROM.
- 10) Define content addressable memories.

### SECTION-B

- 11) Design a 3 bit odd parity generator.
- 12) Minimize the following expression using Q-M method  
$$Y = \sum m (1, 2, 3, 6, 7, 9, 10, 11, 13)$$
- 13) Design SR flip flop using JK flip flop.
- 14) Write a VHDL code for full adder.
- 15) Draw and explain dual slope A/D converter.

### SECTION-C

- 16) Differentiate between various types of ROM.
- 17) Explain FPGA in detail.
- 18) Design universal shift register.

downloaded from  
StudentSuvidha.com