

Total No. of Questions : 8]

[Total No. of Printed Pages : 2

Roll No .....

**MCADD-105**  
**M.C.A. (Integrated), I Semester**  
Examination, June 2020  
**Digital Electronics**  
**Time : Three Hours**

**Maximum Marks : 70**

**Note:** i) Attempt any five questions.

ii) All questions carry equal marks.

1. a) Convert following Decimal Number to Binary
  - i) 25
  - ii) 125
  - iii) 145
  - iv) 51
- b) Convert following Decimal number to octal.
  - i)  $(456)_{10}$  to octal
  - ii)  $(212)_{10}$  to octal
  - iii)  $(100)_{10}$  to octal
  - iv)  $(127)_{10}$  to octal
2. a) Explain the Grey code and BCD numbers.
- b) Discuss application of logical Gates.
3. Explain the following terms:
  - a) Half-Adder
  - b) OR and NOR gate
  - c) De-Morgan's theorem

MCADD-105

PTO

[2]

4. a) Explain the R-S Flip-Flop in detail. What is the Race-Around condition and how it can be eliminated?  
b) Explain briefly the Karnaugh's map and SOP and POS methods.
5. Draw the diagram of Full-Adder and explain it.
6. What is multiplexor and De-multiplexor? Draw the 4:1 multiplexor and explain.
7. a) What is Ripple counter? Draw and explain 2 Bit Ripple-up-counter using negative edge triggered Flip-Flops.  
b) What is MOD10 counter? Explain it.
8. Write short notes on any three.
  - i) TTL circuits
  - ii) Static and Dynamic RAM
  - iii) Shift Registers
  - iv) Decoder

\*\*\*\*\*