

Total No. of Questions : 8]

[Total No. of Printed Pages : 4

Roll No

CS/CT/CO/CI-304-CBGS

B.Tech., III Semester

Examination, June 2020

Choice Based Grading System (CBGS)

CS-304: Digital Systems

CI-304: Digital Circuits and System

Time : Three Hours

Maximum Marks : 70

Note: i) Attempt any five questions.

ii) All questions carry equal marks.

iii) In case of any doubt or dispute the English version question should be treated as final.

1. a) What is Boolean Algebra? Compare it with Karnaugh map.
Also simplify the following expression using k-map. 7

$$y = \bar{A} \bar{B} \bar{C} + \bar{B} \bar{C} + \bar{A} \bar{B}$$

$$y = \bar{A} \bar{B} \bar{C} + \bar{B} \bar{C} + \bar{A} \bar{B}$$

- b) What are the universal Gate? Why we call them universal?
Explain it with examples. 7

CS/CT/CO/CI-304-CBGS

PTO

[2]

2. a) What are the weighted code? Explain any two weighted code. 7
- b) If $X = 111.101$ and $Y = 101.110$. Calculate $x + y$, and $x - y$ and $y - x$ by 2's complement method. 7
3. a) What is the difference between combinational circuit and sequential circuit? Explain. 7
- b) Implement the function
 $f(A, B, C, D) = \sum (0, 1, 5, 7, 10, 14, 15)$ using 8:1 multiplexer. 7
- $f(A, B, C, D) = \sum (0, 1, 5, 7, 10, 14, 15)$
4. a) What is decoder? Explain BCD to decimal decoder. 7
- b) Design a combinational circuit to convert the binary input ABCD to gray code. 7
5. a) Explain synchronous and Asynchronous counter. 7

CS/CT/CO/CI-304-CBGS

Contd...

[3]

b) What is Flip-Flop? Explain Master Slave J-K flip-flop. 7

i

6. a) Write short notes on 7
i) Semiconductor memories
ii) DRAM

b) Draw and explain astable multivibrator? 7

7. a) Implement the following circuit using CMOS logic 7
i) $Y = A \cdot B$
ii) $Y = A + B$

i) $Y = A \cdot B$

ii) $Y = A + B$

b) With a neat diagram, explain the operation of 8 bit successive approximation ADC. 7

8 bit

CS/CT/CO/CI-304-CBGS

PTO

[4]

8. Explain any two

14

- i) Sampling theorem
- ii) PCM
- iii) TTL
- iv) BPSK

downloaded from
StudentSuvidha.com

CS/CT/CO/CI-304-CBGS