

Roll No

EE/EX-3003-CBGS

B.E. III Semester

Examination, December 2020

Choice Based Grading System (CBGS)

Network Analysis

Time : Three Hours

Maximum Marks : 70

- Note:** i) Attempt any five questions.
 ii) All questions carry equal marks.

1. a) Consider the R-C parallel circuit shown in fig. 1 excited by a d.c. current source of 10A. Determine the voltage across the capacitor. Assume the initial voltage across the capacitor as 2V.

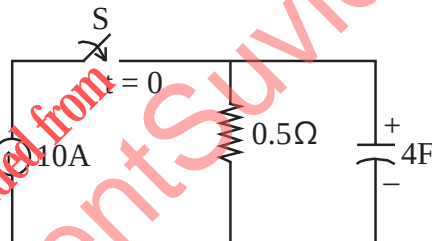


Fig.1

- b) At $t = 0$, S is closed in the circuit of fig.2 find $v_c(t)$ and $i_c(t)$. All initial conditions are zero.

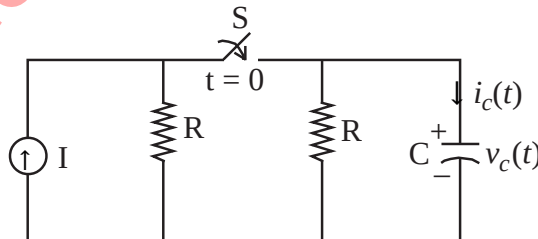


Fig.2

[2]

2. a) Find $i(t)$ for $t > 0$ in the circuit shown in fig. 3 switch S is opened at $t = 0$.

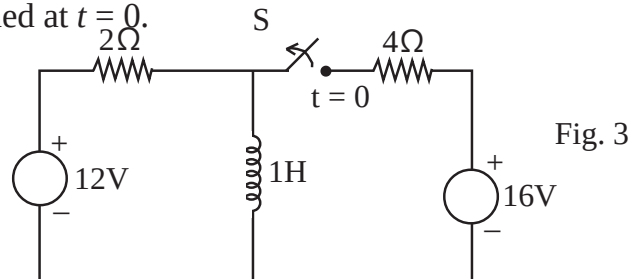


Fig. 3

- b) In the circuit shown in fig. 4, the switch S is closed at $t = 0$ connecting a source e^{-t} to the RC circuit. At $t = 0$ it is observed that the capacitor voltage has the value $v_c(0) = 0.5V$. Determine $v_2(t)$.

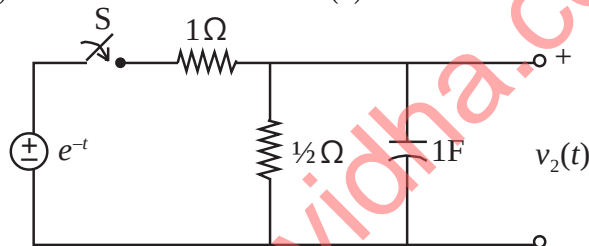


Fig. 4

3. a) Verify reciprocity theorem for the circuit shown in fig.5.

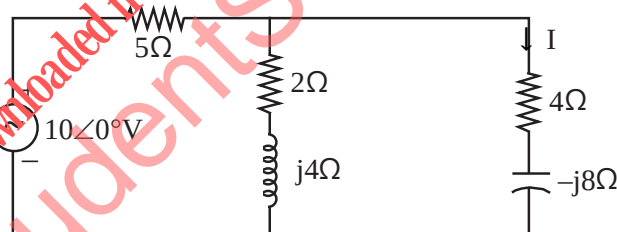


Fig. 5

- b) Find the Thevenin equivalent circuit at terminal AB of the circuit given in fig. 6.

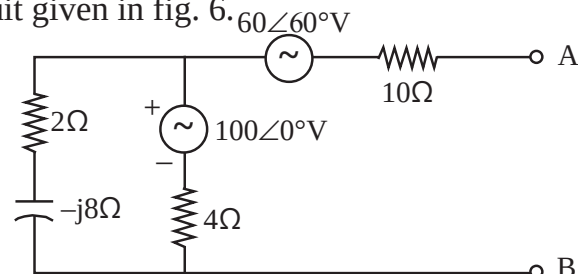


Fig. 6

EE/EX-3003-CBGS

Contd...

[4]

7. a) Obtain the z-parameters of the network shown in Fig. 11

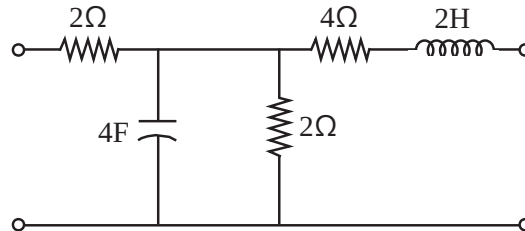


Fig. 11

- b) Determine the z-parameters of the network shown in Fig. 12.

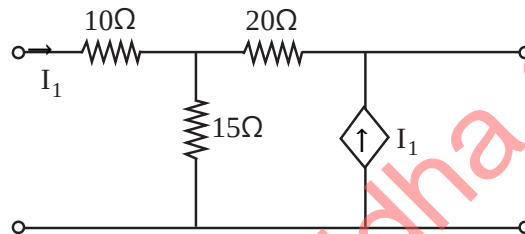


Fig. 12

8. Write short notes on any two of the following:
- Parallel resonance.
 - Initial and final value theorem.
 - Hybrid parameters.

EE/EX-3003-CBGS